

4-bit Counter by using JK Flip-Flops

— David —

Nov. 27, 2025



Contents

- **Sequential Logic Circuits**
 - SR Latch and JK Flip-Flop
- **Simulation**
 - LTspice and R-2R DAC
 - ModelSim
- **Experiment**
 - Altera DE2-115 and switch debouncing


Sequential Logic Circuits

- Sequential Logic
 - SR Latch
 - JK Flip-Flop
-


Combinational & Sequential Circuits




Combinational Circuit

 

Full Adder

 

Sequential Circuit

 

SR Flip Flop


Combinational & Sequential Circuits

Combinational circuits compute functions where the output is a direct function of present inputs only; they contain no storage elements and have no notion of past inputs. **Sequential circuits** include memory elements (flip-flops, latches) so outputs depend on both current inputs and previously stored states, making them inherently time-dependent and stateful.


| Attribute | Combinational | Sequential |
|--------------------|-----------------------------|---------------------------------------|
| Output depends on | Current inputs only | Current inputs and past state |
| Contains memory | No | Yes (flip-flops, latches) |
| Time behavior | Time-independent | Time-dependent (clocked/asynchronous) |
| Typical use | Arithmetic, logic functions | Counters, controllers, registers |
| Verification focus | Boolean correctness | State transitions and timing |

(NOR-based) SR Latch

 - A NOR-based S-R latch is the simplest **bistable** circuit built from two cross-coupled NOR gates; it stores a single binary state and is changed by the **Set (S)** and **Reset (R)** inputs.
- Key behavior:
 - S=1 sets Q=1,
 - R=1 resets Q=0,
 - and S=R=1 is an invalid/forbidden condition.




| S | R | Q | \bar{Q} |
|---|---|-------|-----------|
| 0 | 0 | latch | latch |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

 



| S | R | Q_{n+1} | \bar{Q}_{n+1} | Operation |
|----------|----------|-----------|-----------------|--------------------------------------------------|
| V_{OH} | V_{OL} | V_{OH} | V_{OL} | M1 and M2 on, M3 and M4 off |
| V_{OL} | V_{OH} | V_{OL} | V_{OH} | M1 and M2 off, M3 and M4 on |
| V_{OL} | V_{OL} | V_{OH} | V_{OL} | M1 and M4 off, M2 on, or M1 and M4 off, M3 on |
| V_{OL} | V_{OL} | V_{OL} | V_{OH} | |

Source:
<https://www.allaboutcircuits.com/textbook/digital/chpt-10/s-r-latch/>
https://www.tutorialspoint.com/vlsi_design/vlsi_design_sequential_mos_logic_circuits.htm
https://course.cutm.ac.in/wp-content/uploads/2020/06/Lect28_DIC.pdf

(NAND-based) SR Latch

 


| S | R | Q_{n+1} | \bar{Q}_{n+1} | Operation |
|---|---|-----------|-----------------|-------------|
| 0 | 0 | 1 | 1 | not allowed |
| 0 | 1 | 1 | 0 | set |
| 1 | 0 | 0 | 1 | reset |
| 1 | 1 | Q_n | \bar{Q}_n | hold |

  

NAND SR latch responds to active low input signals whereas NOR SR latch responds to active high input signals.

Switch Bounce


- Mechanical contacts physically bounce when they close or open, producing a train of short pulses that digital logic can interpret as many presses.
- Typical failure modes and what to watch for:
 - **Both S and R briefly asserted** during a transition can produce an invalid or metastable state in some SR implementations (especially simple NAND/NOR cross-coupled latches).
 - **Glitches from slow edges** can still trigger logic if the latch inputs are noisy or if there's no hysteresis.
 - **Power-up undefined state** — an SR latch may power up in either state unless you provide a defined reset.

 

Source:

<https://www.clarvis.co.uk/Electronics/Practical-Circuits/Switch-bounce.html>

Switch Bounce: Solution

 


Solution B Schmitt Trigger


- A Add simple **RC** timing before the SR latch
- B Use a **Schmitt** trigger first
- C Use a **one-shot** or **monostable** to generate a single clean pulse
- D Replace SR latch with a **D flip-flop** sampled by a periodic clock
- E Software debounce: Read the raw input and require it to be **stable** for a **fixed time** (e.g., 5–50 ms) before accepting the change.

Source:



 
<https://www.geeksforgeeks.org/digital-logic/switch-debounce-in-digital-circuits/>
<https://www.clarvis.co.uk/Electronics/Practical-Circuits/Switch-bounce.html>



Solution C 555 Monostable Circuit

 

(NOR-based) Gated SR Flip-flop

   

Source:

https://www.electronics-tutorials.ws/sequential/seq_1.html

https://course.cutm.ac.in/wp-content/uploads/2020/06/Lect28_DIC.pdf




(NOR-based) JK Flip-Flop

The JK flip-flop is a gated SR flip-flop with an additional clock input circuitry that prevents the invalid output condition when both inputs S and R are equal to logic level "1".

Truth Table

| CLK | J | K | Q_{n+1} |
|-----|---|---|-----------|
| ↑ | 0 | 0 | Q_n |
| ↑ | 0 | 1 | 0 |
| ↑ | 1 | 0 | 1 |
| ↑ | 1 | 1 | Q_n' |


Symbol

   


Source:

https://course.cutm.ac.in/wp-content/uploads/2020/06/Lect28_DIC.pdf
<https://www.allaboutelectronics.org/jk-flip-flop-explained-race-around-condition-in-jk-flip-flop-jk-flip-flop-truth-table-excitation-table-and-timing-diagram/>

JK Flip-Flop

 

 - Sometimes JK flip-flops contain an additional set and reset pin. The set and reset pins work as preset and clear to **initialize** the flip-flop.
- Preset (**PRE**) and Clear (**CLR**): Asynchronous inputs used to directly set or reset the flip-flop regardless of the clock.




| Preset | Clear | CLK | J | K | Q | Q(not) |
|--------|-------|-----|---|---|----|--------|
| X | 1 | X | X | X | 0 | 1 |
| 1 | X | X | X | X | 1 | 0 |
| 0 | 0 | ↑ | 1 | 0 | 1 | 0 |
| 0 | 0 | ↑ | 0 | 1 | 0 | 1 |
| 0 | 0 | ↑ | 1 | 1 | 1* | 0 |
| 0 | 0 | ↑ | 0 | 0 | 1~ | 0 |

Source:


<https://www.ema-eda.com/ema-resources/blog/jk-flip-flop-spice-model-explained/>

<https://compraco.com.br/en/blogs/tecnologia-e-desenvolvimento/tutorial-vhdl-17-projete-um-flip-flop-jk-com-preset-e-clear-usando-vhdl>

4-bit Synchronous Up Counter

 

 Source: <https://www.electronics-lab.com/article/synchronous-counter/>



Simulation

- LTspice and DAC
 - ModelSim
-

Simulation

- **LTspice and DAC**
- ModelSim


LTspice



- **SPICE**, standing for "**Simulation Program with Integrated Circuit Emphasis**," is a computer program that simulates the behavior of electronic circuits, enabling engineers to analyze and test them virtually before building them physically.
- **LTspice** is a free **SPICE simulator** software from **Analog Devices** that is used to design, test, and analyze electronic circuits before building physical prototypes.

0101 Library
 
<http://ltspicegoodies.ltwiki.org/0101.php>




JKFLOP

J-K flip-flop.


- 'J', 'K', 'CLK' are floating inputs.
- 'PRE', 'CLR' are the set and rese pins, respectively, with $1G\Omega$ internal pulldown.
- The ground pin is 'RTN' and **cannot be left floating!**

Parameters:

| | | |
|----------------|-----|----------------------------------------------------------------------------------|
| Vhigh,Vlow | [V] | Output logic levels, defaults <1,0> |
| <u>Hidden:</u> | | |
| td | [s] | LTspice's specific for A-devices (should not be set null!), default 10n |

 
 
```
PULSE(0 1 0 1n 1n 20n 40n)  
.tran 10u
```




4-bit Counter in LTspice

Discussion (i)

Flip-Flop Toggling in V(q1):

 The least significant bit (LSB) flip-flop toggles its state with every active edge.




Digital-to-Analog Converter (DAC)

- To observe an analog signal, I input a digital signal (a series of 0s and 1s) into the Digital-to-Analog Converter (DAC). The DAC then converts this digital data into a corresponding analog voltage or current, which is the output signal.
- Types of DACs
 - **R-2R ladder** and weighted-resistor DACs
 - **Current-steering** and flash DACs
 - **Sigma-Delta ($\Delta\Sigma$)** DACs
 - **PWM** (pulse-width modulation) DACs

Types of DACs


- **R-2R ladders** implement binary weighting with only two resistor values, making them simple and area-efficient for moderate resolutions, but they rely on tight resistor matching and low switch error for accuracy.
- **Current-steering (flash) DACs** use many parallel current sources switched in one clock cycle to achieve very high conversion rates; they are the go-to choice when speed is the primary requirement, at the cost of higher power and silicon area.
- **Sigma-delta ($\Delta\Sigma$) DACs** trade instantaneous bandwidth for in-band performance by oversampling the signal and shaping quantization noise out of the band of interest; a digital filter and analog reconstruction recover a high-resolution analog output, making them ideal for audio and precision low-frequency applications.
- **PWM DACs** are commonly used in microcontrollers: the desired amplitude is encoded as pulse duty cycle and a simple RC or active low-pass filter smooths the waveform; this approach is inexpensive and flexible but requires careful filtering and clock stability to control ripple and effective resolution.

R-2R DAC

 


<https://www.electronics-tutorials.ws/combination/r-2r-dac.html>

Current steering DAC

 


https://www.researchgate.net/figure/Current-steering-DAC-intended-for-high-speed-applications-A-six-bit-DAC-has-been_fig12_3074734

Sigma-delta DAC

 


<https://www.moon-audio.com/blogs/expert-advice/dac-types-deciphered>

PWM DAC

 

<https://www.edntaiwan.com/20200210ta31-pwm-dac-settles-in-one-period-of-the-pulse-train/>

| Architecture | Key concept | Typical speed | Typical resolution | Strengths / Limitations |
|------------------------------------------------|------------------------------------------------------------------------------------|----------------------------|---------------------------------------------------|-----------------------------------------------------------------------------------------------------------------|
| R-2R ladder | resistor network using only R and 2R values to weight bits | low-moderate | up to ~16 bits (practical) | Strengths: simple, compact; Limitations: resistor matching limits high precision |
| Current-steering / Flash | parallel switched current sources produce output in one cycle | very high (GHz class) | low-moderate (6-14 bits common) | Strengths: ultra-fast; Limitations: area/power scale with resolution |
| Sigma-Delta ($\Delta\Sigma$) | oversampling + noise shaping; digital modulator + analog reconstruction | low-moderate (bandlimited) | very high effective resolution (24+ bits in band) | Strengths: excellent linearity and SNR in band; Limitations: latency, not for wideband RF |
| PWM DAC | encode amplitude as duty cycle of pulse train; low-pass filter reconstructs analog | low (timer limited) | limited by timer and filter (8-16 bits practical) | Strengths: very low cost, MCU-friendly; Limitations: needs filtering, switching ripple and jitter |

 


- The binary set $\{q1, q2, q3, q4\}$ is collected and now represented by the analog output **Vout**.
- When we count from 1 to 15, the reading (**Vout**) will change from -15 to -150 mV.

4-bit Counter in LTspice

Discussion (ii)

 
Rollover: When the 4-bit counter reaches its maximum value of 1111 (decimal 15) and receives another increment request, the MSB (the '1' in 10000) is discarded, and the counter rolls over, resetting its value back to 0000.



Simulation

- LTspice and DAC
- **ModelSim**

Write VHDL to implement JK Flip-Flops

 

Netlist of jk_ff


```
24 library ieee;
25 use ieee.std_logic_1164.all;
26
27 entity jk_ff is
28     port (
29         J       : in  std_logic;
30         K       : in  std_logic;
31         Clock   : in  std_logic;
32         nReset  : in  std_logic;
33         Q       : out std_logic
34     );
35 end entity jk_ff;
36
37 architecture rtl of jk_ff is
38     signal Q_reg : std_logic;
39 begin
40     process(nReset, Clock)
41     begin
42         if nReset = '0' then
43             Q_reg <= '0';
44         elsif rising_edge(Clock) then
45             if (J = '1' and K = '1') then
46                 Q_reg <= not Q;
47             elsif (J = '1' and K = '0') then
48                 Q_reg <= '1';
49             elsif (J = '0' and K = '1') then
50                 Q_reg <= '0';
51             end if;
52         end if;
53         Q <= Q_reg;
54     end process;
55 end architecture rtl;
```

Write VHDL to 4-bit Counter by using JK Flip-Flops

```
28  library ieee;
29  use ieee.std_logic_1164.all;
30
31  entity jk_4bit_counter is
32      port (
33          Clock : in  std_logic;
34          nReset : in  std_logic; -- active low reset
35          Enable : in  std_logic; -- count when '1'
36          Q      : out std_logic_vector(3 downto 0)
37      );
38  end entity jk_4bit_counter;
```

```
40  architecture rtl of jk_4bit_counter is
41      -- internal signals for J and K
42      signal q_reg : std_logic_vector(3 downto 0) := (others => '0');
43      signal J     : std_logic_vector(3 downto 0);
44      signal K     : std_logic_vector(3 downto 0);
45  begin
46
47      -- J assignments for toggle-style ripple counter
48      J(0) <= Enable;
49      J(1) <= Enable and q_reg(0);
50      J(2) <= Enable and q_reg(0) and q_reg(1);
51      J(3) <= Enable and q_reg(0) and q_reg(1) and q_reg(2);
52
53      -- K equals J for toggle behavior
54      K <= J;
55
56      -- Instantiate four jk_ff components using a generate loop
57      gen_bits : for i in 0 to 3 generate
58          jk_inst : entity work.jk_ff
59              port map (
60                  J     => J(i),
61                  K     => K(i),
62                  Clock => Clock,
63                  nReset => nReset,
64                  Q     => q_reg(i)
65              );
66      end generate gen_bits;
67
68      -- output assignment
69      Q <= q_reg;
70
71  end architecture rtl;
```


VHDL testbench

 

```

35 library ieee;
36 use ieee.std_logic_1164.all;
37 use ieee.numeric_std.all;
38
39 entity tb_jk_4bit_counter is
40 end entity tb_jk_4bit_counter;
41
42 architecture sim of tb_jk_4bit_counter is
43     -- DUT signals
44     signal Clock : std_logic := '0';
45     signal nReset : std_logic := '1'; -- active low
46     signal Enable : std_logic := '0';
47     signal Q : std_logic_vector(3 downto 0);
48
49     constant CLK_PERIOD : time := 20 ns; -- 50 MHz
50 begin
51
52     -- Instantiate the device under test
53     uut: entity work.jk_4bit_counter
54         port map (
55             Clock => Clock,
56             nReset => nReset,
57             Enable => Enable,
58             Q => Q
59         );
60
61     -- Clock generator
62     clk_proc : process
63     begin
64         while true loop
65             Clock <= '0';
66             wait for CLK_PERIOD / 2;
67             Clock <= '1';
68             wait for CLK_PERIOD / 2;
69         end loop;
70     end process clk_proc;
71
72     -- Monitor process: print Q on each rising edge
73     monitor_proc : process(Clock)
74     begin
75         if rising_edge(Clock) then
76             report "At time " & time'image(now) & " Q = " & integer'image(to_integer(
77                 Q));
78         end if;
79     end process monitor_proc;
80
81 end architecture sim;



```

```

-- Stimulus process
73 stim_proc : process
74 begin
75     -- initial asynchronous reset asserted
76     nReset <= '0';
77     Enable <= '0';
78     wait for 25 ns;
79
80     -- release reset
81     nReset <= '1';
82     wait for 15 ns;
83
84     -- start counting
85     Enable <= '1';
86     report "Enable asserted, counting should start" severity note;
87
88     -- let it count for a number of clock cycles (observe wrap-around)
89     wait for 10 * CLK_PERIOD; -- 10 clock cycles
90
91     -- disable counting (hold)
92     Enable <= '0';
93     report "Enable deasserted, counter should hold" severity note;
94     wait for 5 * CLK_PERIOD;
95
96     -- re-enable counting
97     Enable <= '1';
98     report "Enable reasserted, counting resumes" severity note;
99     wait for 8 * CLK_PERIOD;
100
101     -- assert asynchronous reset again to test clear
102     nReset <= '0';
103     report "Asserting asynchronous reset (active low)" severity note;
104     wait for 7 ns; -- asynchronous, so can be asserted between clocks
105     nReset <= '1';
106     report "Releasing asynchronous reset" severity note;
107     wait for 4 * CLK_PERIOD;
108
109     -- final hold and finish
110     Enable <= '0';
111     wait for 2 * CLK_PERIOD;
112
113     report "End of testbench" severity note;
114     -- stop simulation
115     assert false report "Simulation finished" severity failure;
116     wait;
117 end process stim_proc;

```

VHDL Testbench

  

Discussion

- **Flip-Flop Toggling:** The least significant bit (LSB) flip-flop toggles its state with every active edge.
- **Rollover:** When the 4-bit counter reaches its maximum value of 1111 (decimal 15) and receives another increment request, the MSB (the '1' in 10000) is discarded, and the counter rolls over, resetting its value back to 0000.
- **nReset:** An active-high input that, when asserted (time = 283 ns), clears the counter to zero.

Experiment

- DE2-115
- Debouncing

Write VHDL to show the value on 7-segment display

```
22  entity hex7seg_display is
23      port(
24          clk          : in  std_logic;
25          rst_n        : in  std_logic;
26          sum_number   : in  std_logic_vector(3 downto 0);
27          hex0_a       : out std_logic;
28          hex0_b       : out std_logic;
29          hex0_c       : out std_logic;
30          hex0_d       : out std_logic;
31          hex0_e       : out std_logic;
32          hex0_f       : out std_logic;
33          hex0_g       : out std_logic
34      );
35  end entity;
```

```
74  with digit select
75  seg_pat <=
76      "000001" when "0000", -- 0: a b c d e f ON, g OFF
77      "1001111" when "0001", -- 1
78      "0010010" when "0010", -- 2
79      "0000110" when "0011", -- 3
80      "1001100" when "0100", -- 4
81      "0100100" when "0101", -- 5
82      "0100000" when "0110", -- 6
83      "0001111" when "0111", -- 7
84      "0000000" when "1000", -- 8: all segments ON
85      "0000100" when "1001", -- 9
86      "0001000" when "1010", -- A
87      "1100000" when "1011", -- b
88      "0110001" when "1100", -- C
89      "1000010" when "1101", -- d
90      "0110000" when "1110", -- E
91      "0111000" when "1111", -- F
92      "1111111" when others; -- default: all segments OFF (blank)
93
98  hex0_a <= seg_pat(6);
99  hex0_b <= seg_pat(5);
100  hex0_c <= seg_pat(4);
101  hex0_d <= seg_pat(3);
102  hex0_e <= seg_pat(2);
103  hex0_f <= seg_pat(1);
104  hex0_g <= seg_pat(0);
```

Experiment on Altera DE2-115

ISSUE:

The **switch bounce** occurs!



software/hardware debouncing: timer + 2-stage synchronizer

<software> timer filter

- `stable0` holds the current debounced level. A counter `cnt` increments only when the synchronized input `sync1` differs from `stable0`. If `sync1` equals `stable0`, the counter is cleared. When `cnt` reaches `THRESH-1`, `stable0` is updated to `sync1` and the counter resets.

<hardware> two-stage synchronizer

- `sync0` and `sync1` sample `raw_btn` on consecutive clocks to avoid metastability and bring the asynchronous input into the clock domain.

Timing and THRESH

The constant `THRESH` is computed as:

$$\text{THRESH} = \frac{\text{CLOCK_FREQ_HZ}}{1000} \cdot \text{DEBOUNCE_MS}$$

For the default generics (50 MHz clock, 20 ms debounce) that equals:

$$\text{THRESH} = \frac{50\,000\,000}{1000} \cdot 20 = 1\,000\,000 \text{ clock cycles.}$$

So the input must remain steady for ~1,000,000 clock cycles (~20 ms) before the change is accepted.




Write VHDL to implement button_debouncer

```
46  entity button_debouncer is
47      generic (
48          CLOCK_FREQ_HZ : natural := 50_000_000;
49          DEBOUNCE_MS   : natural := 20;
50          CNT_WIDTH     : natural := 20
51      );
52  port (
53      clk      : in  std_logic;
54      rst_n    : in  std_logic;
55      raw_btn  : in  std_logic; -- asynchr
56      db_level : out std_logic; -- debounc
57      db_pulse : out std_logic  -- single-
58  );
59  end entity;
--
72  -- 2-stage synchronizer to avoid metastability
73  process(clk)
74  begin
75      if rising_edge(clk) then
76          if rst_n = '0' then
77              sync0 <= '0';
78              sync1 <= '0';
79          else
80              sync0 <= raw_btn;
81              sync1 <= sync0;
82          end if;
83      end if;
84  end process;
86  -- initial hold-off counter after reset: keep c
87  process(clk)
88  begin
89      if rising_edge(clk) then
90          if rst_n = '0' then
91              init_cnt <= (others => '0');
92              init_done <= '0';
93          else
94              if init_done = '0' then
95                  if init_cnt = THRESH - 1 then
96                      init_done <= '1';
97                      init_cnt <= (others => '0');
98                  else
99                      init_cnt <= init_cnt + 1;
100                 end if;
101             end if;
102         end if;
103     end if;
104 end process;
106  -- debounce counter: require sync1 to
107  process(clk)
108  begin
109      if rising_edge(clk) then
110          if rst_n = '0' then
111              stable0 <= '0';
112              cnt <= (others => '0');
113          elsif init_done = '0' then
114              -- during initial hold-off keep
115              stable0 <= '0';
116              cnt <= (others => '0');
117          else
118              -- normal debounce operation
119              if sync1 = stable0 then
120                  cnt <= (others => '0');
121              else
122                  if cnt = THRESH - 1 then
123                      stable0 <= sync1;
124                      cnt <= (others => '0');
125                  else
126                      cnt <= cnt + 1;
127                  end if;
128              end if;
129          end if;
130      end if;
131  end process;
```

Write VHDL to implement button_debouncer

(block design)

 

Experiment on Altera DE2-115



Conclusions

- Counter (LSB & MSB)
 - LTspice & ModelSim
 - R-2R DAC
 - Switch Debouncing
-

Conclusions

- The flip-flop toggling and rollover are both observed in our simulators (LTspice and ModelSim) and experiments (DE2-115).
- The R-2R ladder is implemented with two resistor values to convert binary digital signals into an analog voltage.
- A two-stage synchronizer with some timer filtering can debounce a pushbutton.

4-bit counter by using JK flip-flops

**If you have any feedback,
please contact me at**

— twwang97@gmail.com —



twwang97

Electronics and AI Training Program (3rd session in 2025)

Thanks for your attention



NYCU

國立陽明交通大學



陽明交大雷射系統研究中心